




Riya Gola 2300320120201

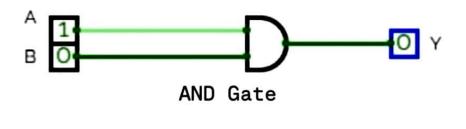


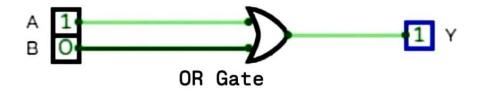

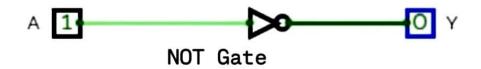


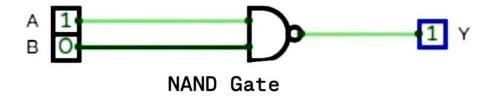


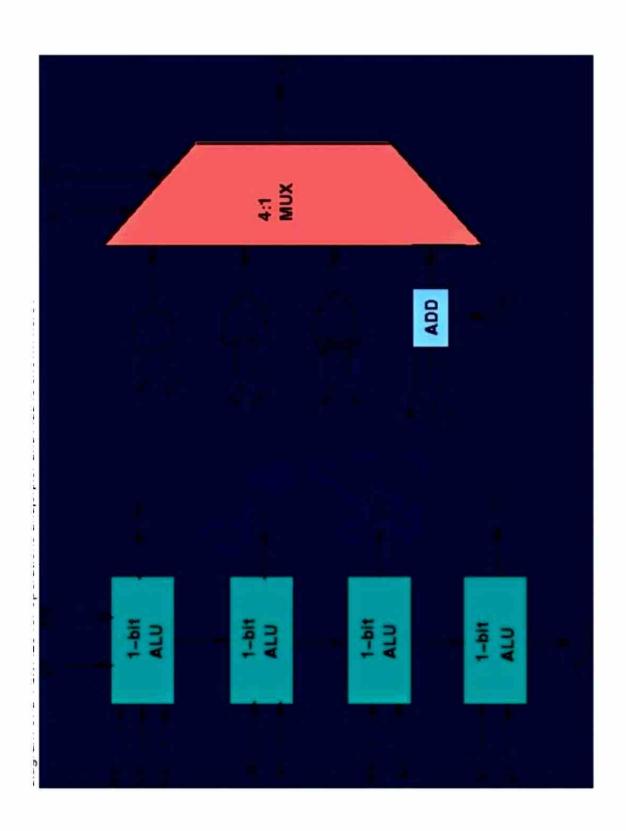

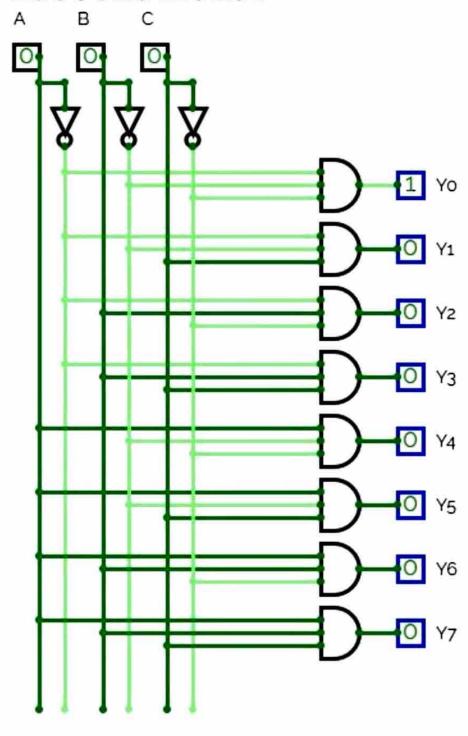



3-8 Line Decoder

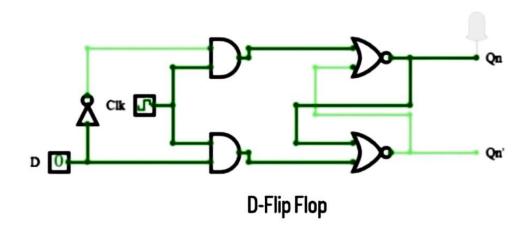

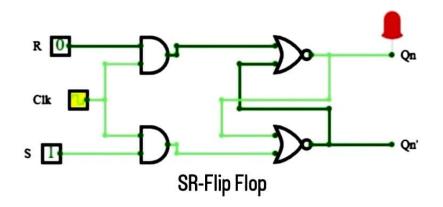


Riya Gola 2300320120201

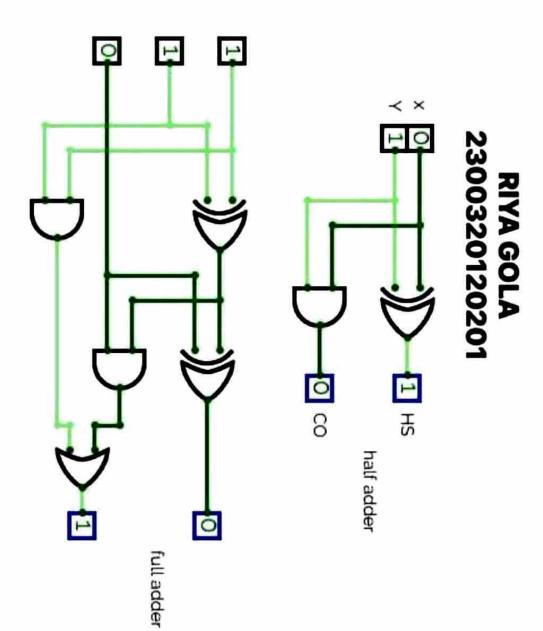


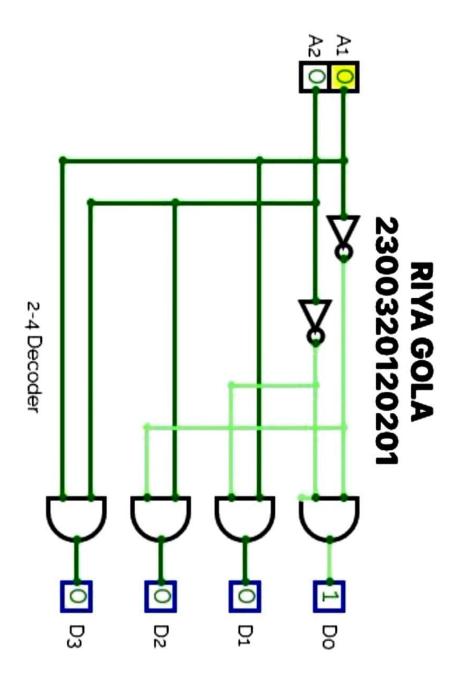


RIYA JAIN 2300320120202

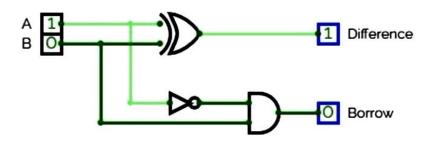



Half Substractor

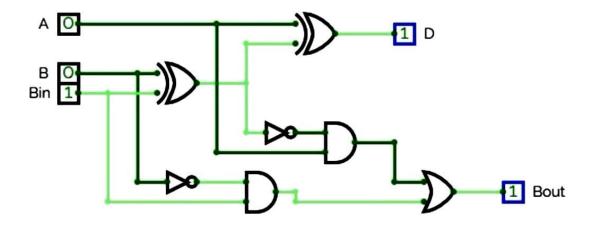


Full Substractor

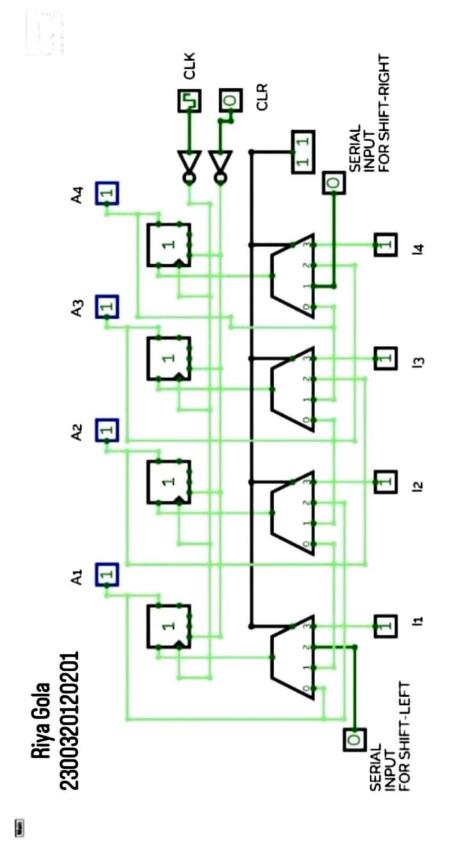


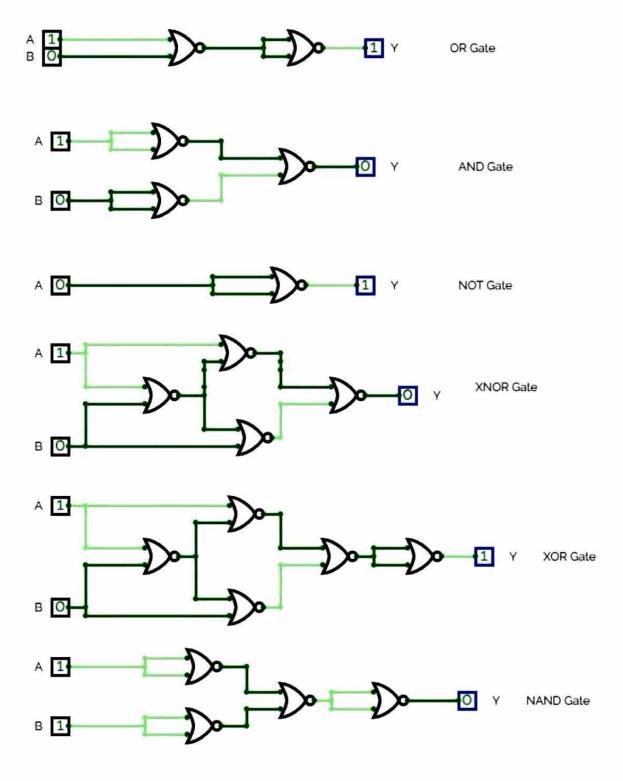

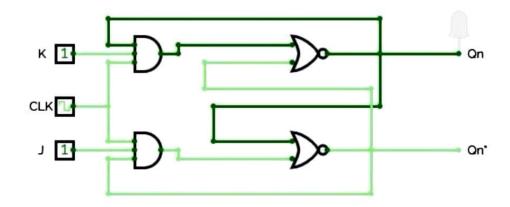


JK Flip Flop

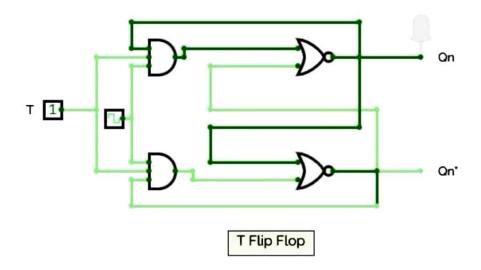

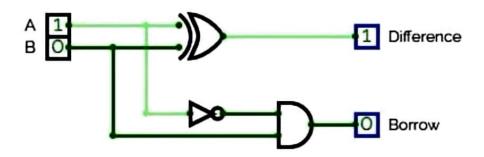



Half Substractor

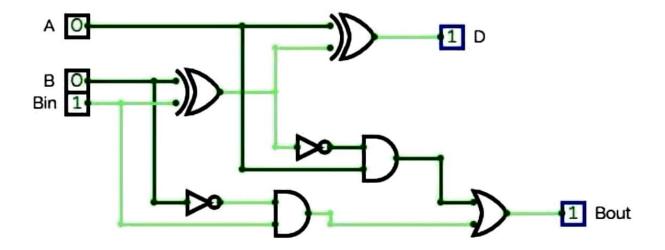


Full Substractor


Riya Gola 2300320120201

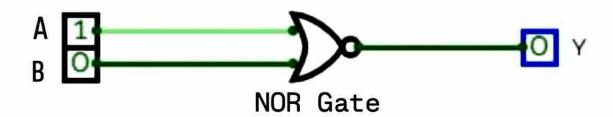

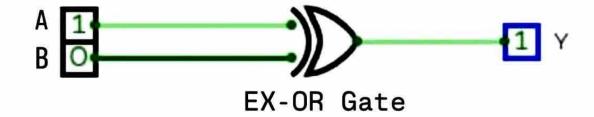



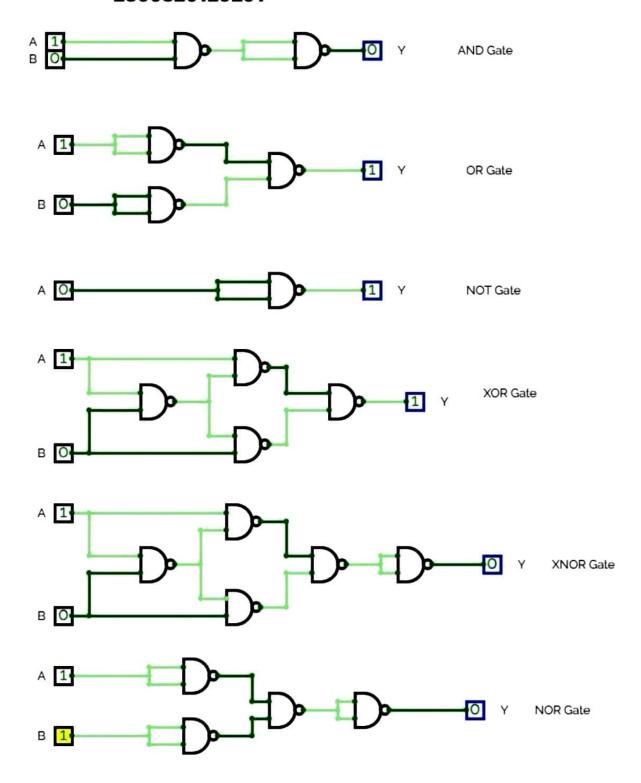

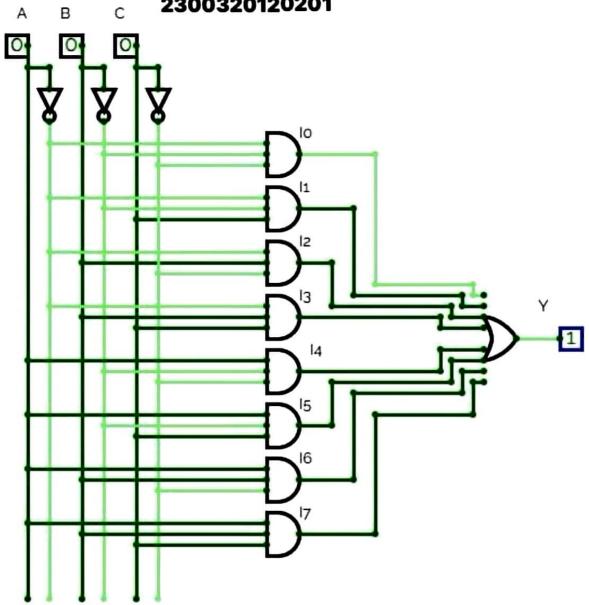

8:1 MULTIPLEXER

